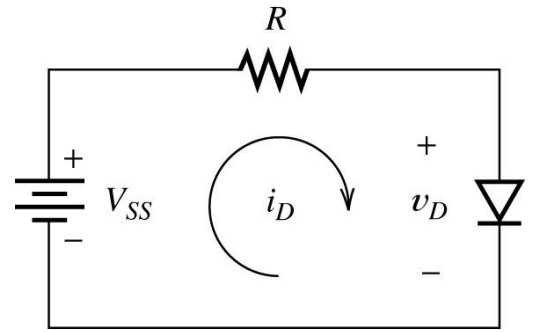


LAST NAME

FIRST NAME


Problem 1

- A) Given $R=300\ \Omega$ & $V_{ss}=6.0\text{ V}$ Draw the DC load line.
- B) Use graphical method to obtain the Q point and write down the approximate values for I_{DQ} and V_{DQ} .
- C) Use graphical method to obtain the value of r_d at the Q point.
- D) Repeat A), B), and C) for $V_{ss}=1.5\text{ V}$.



ANSWERS (draw tangents as accurately as possible)

V_{ss} (V)	V_{DQ} (V)	I_{DQ} (mA)	r_{dQ} (Ω)
6.0	1.2	16.0	15.6
1.5	0.8	2.5	80.0

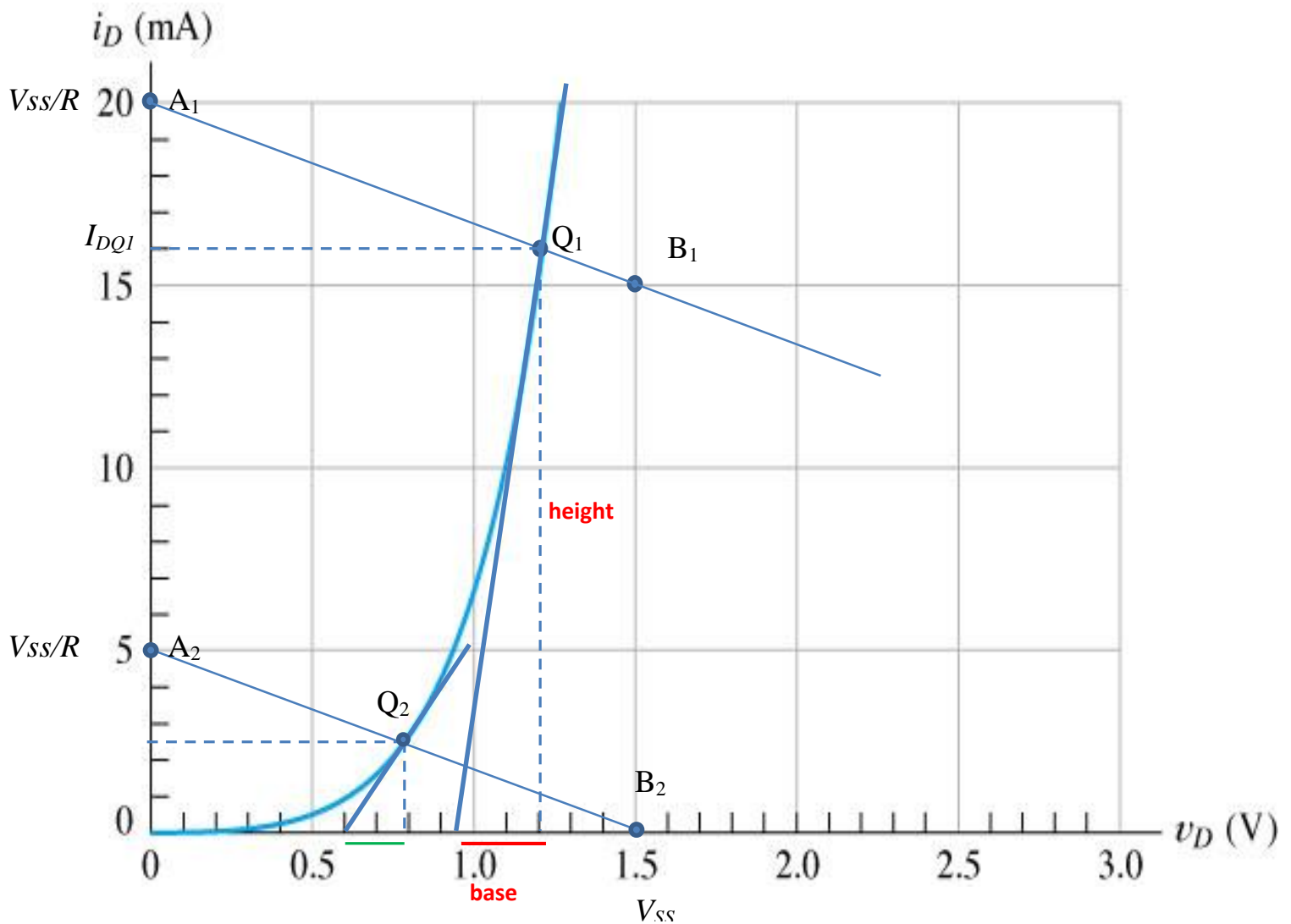

LAST NAME

FIRST NAME

Problem 1 continued

Unit convention : $[R] = k\Omega$ $[i] = mA$ $[v] = V$

Load Lines :

$KVL \Rightarrow v_D = V_{SS} - Ri_D$ This represents a straight line in the $v_D - i_D$ space (*load line*)

Drawing Load Lines :

Find two points on the line by choosing two values of i_D and the corresponding v_D values.

Case 1: $V_{SS} = 6V : v_D = 6 - 0.3i_D$.

For example A_1 : choose $i_D = 20 \Rightarrow v_D = 0$ B_1 : choose $i_D = 15 \Rightarrow v_D = 1.5$

Case 2: $V_{SS} = 1.5V : v_D = 1.5 - 0.3i_D$.

For example A_2 : choose $i_D = 0 \Rightarrow v_D = 1.5$ B_2 : choose $v_D = 0 \Rightarrow i_D = 5$

Q - point : Interception of load line with Diode IV curve

Dynamic Resistance : $r_{dQ} = \frac{1}{\text{slope of tangent}} = \frac{\text{triangle base}}{\text{triangle height}}$


Case 1: $r_{dQ} = \frac{0.25 V}{16 mA} = 15.6\Omega$ Case 2: $r_{dQ} = \frac{0.2 V}{2.5 mA} = 80\Omega$

LAST NAME

FIRST NAME

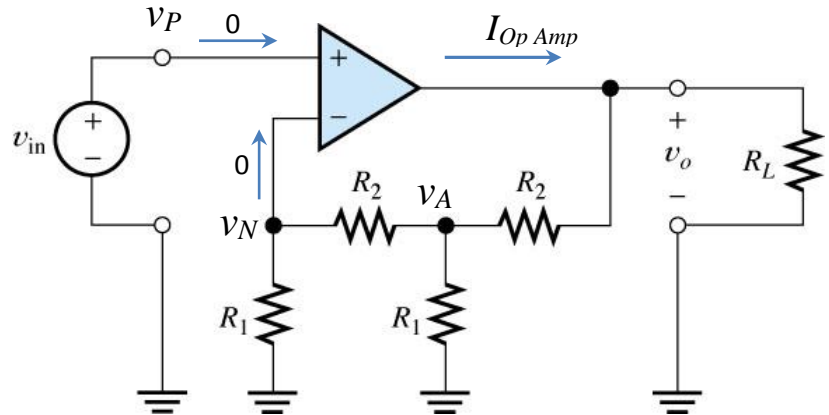Problem 2

Op Amp input resistance is ∞ , output resistance is 0, and open loop gain is ∞ and the power supplies are at +10 and -10 V. $R_1=4\text{ k}\Omega$, $R_2=2\text{ k}\Omega$, and $R_L=2\text{ k}\Omega$. $v_{in}=2\text{ V}$. Find v_o .



Solution:

Assume Op Amp is operating in Linear Region *then* $v_N = v_P$

$$\therefore v_N = 2V$$

Node Voltage Equations

$$\begin{cases} \frac{v_N}{R_1} + \frac{v_N - v_A}{R_2} = 0 & \Rightarrow \frac{2}{4} + \frac{2 - v_A}{2} = 0 \Rightarrow 2 + 4 - 2v_A = 0 \Rightarrow v_A = 3V \\ \frac{v_A}{R_1} + \frac{v_A - v_N}{R_2} + \frac{v_A - v_o}{R_2} = 0 & \Rightarrow \frac{3}{4} + \frac{3 - 2}{2} + \frac{3 - v_o}{2} = 0 \Rightarrow 3 + 2 + 6 - 2v_o = 0 \Rightarrow v_o = 5.5 V \end{cases}$$

Note that $-10 < 5.5 < +10 \Rightarrow -10 < v_o < +10 \Rightarrow$ **Original Assumption IS valid.**

$$I_{Op\ Amp} = \frac{v_o - v_A}{R_2} + \frac{v_o}{R_L} \Rightarrow I_{Op\ Amp} = \frac{5.5 - 3}{2} + \frac{5.5}{2} = 4\text{ A}$$